

**JAYPEE UNIVERSITY OF ENGINEERING & TECHNOLOGY, GUNA**  
**DEPARTMENT OF COMPUTER SCIENCE & ENGINEERING**

**Course: Computer Organization & Architecture Lab**

**Course Code: CS208/18B17CI474**

**B. Tech. (CSE IV/VI Sem.)**

**Experiment # 4**

**Aim: Design of logic circuits using mux, encoder and seven segment displays.**


**Exercise#1:** Design full adder using **in-built block** of (i) 4:1 multiplexer with initial carry as input line and, (ii) 8:1 multiplexer.

**Exercise#2:** Design a logic circuit (using **in-built block** of priority encoder to identify whether the input octal number is even, odd or prime. Use one hex display to show input octal digit and a seven segment display at output which display 'E', 'O' and 'P' if input octal number is even, odd and prime respectively.

**Design Steps:**

- Find truth table with three inputs and three outputs.
- Derive four Boolean expressions for outputs using K-map.
- Implement the logic diagram as per derived Boolean expression and verify it.
- Add one hex display at input.
- Obtain truth table with three inputs and seven outputs for a seven segment logic circuit and derive seven Boolean expressions..
- Connect a seven segment at output as per the derived Boolean expressions.

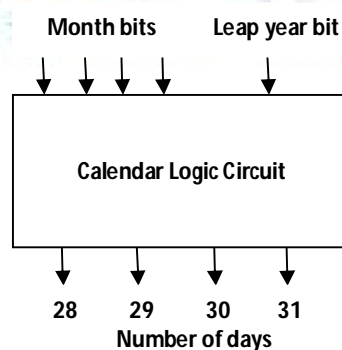
**Exercise#3:** Design calendar logic circuit to show the number of days in a given month. Display input month and leap year using two **hex displays** and number of days in outputs using **two seven segment displays** (two displays for each output).



**Design Steps:**

- Find truth table with five inputs and four outputs.
- Derive four Boolean expressions for outputs using K-map.
- Implement the logic diagram as per derived Boolean expression and verify it.
- Derive Boolean expressions for both the segments and make the connection in seven segments at output as per the obtained Boolean expressions.

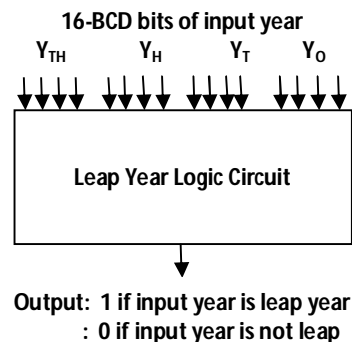**Exercise#4:** Design logic circuit to determine whether the input year is leap year or not. Use **four hex displays** to show four decimal digits of input year and **one hex display** to show output.



Example: input year 1986 will have 16-BCD bits as following:

$Y_O$ : BCD bits for ones place digit 6 = 0110

$Y_T$ : BCD bits for tens place digit 8 = 1000

$Y_H$ : BCD bits for hundreds place digit 9 = 1001

$Y_{TH}$ : BCD bits for thousands place digit 1 = 0001

**Design concepts to derive Boolean expression for leap year:-**

- All years ending with 00, 04, 08, 12, 16, 20, etc. are divisible by 4 and,
  - a. If tens digit is even ( $Y_{T0} = 0$ ), and the ones digit is 0, 4, or 8.
  - b. If tens digit is odd ( $Y_{T0} = 1$ ), and the ones digit is 2 or 6.
  - c. Digits with values of 10 to 15 will never be used.

Using above three concepts, derived Boolean expression for  $D4 = \overline{Y_{T0}} \overline{Y_{O1}} \overline{Y_{O0}} + Y_{T0} Y_{O1} \overline{Y_{O0}}$ .

- All years ending with digits 00 will be divisible by 100. It means lower eight bits ( $Y_O$  and  $Y_T$ ) will be always 0. Therefore, Boolean expression for the year divisible by 100 is  $D100 = \overline{Y_T} \cdot \overline{Y_O}$ .
- All years which are divisible by 4 (**applied to the thousands and hundreds digits**) and 100 both will be divisible by 400. Therefore, Boolean expression for the year divisible by 400 is  $D400 = D4 \cdot D100$ .
- All years which are **divisible by 4 but not by 100** or **divisible by 400** are the leap years. Therefore, final Boolean expression to determine leap year =  $D4 \cdot \overline{D100} + D400$ .